

# ASSIGNMENT-1

D. Siva Krishna  
r170582@rguktrkv.ac.in  
IITH - Future Wireless Communications (FWC)

19-09-2022

## Contents

<b>1 Introduction</b>	<b>1</b>
1.1 7474 IC: . . . . .	1
1.2 Arduino: . . . . .	1
<b>2 Components</b>	<b>1</b>
<b>3 PIN Diagram</b>	<b>1</b>
<b>4 Truth Table</b>	<b>1</b>
<b>5 Circuit Diagram</b>	<b>1</b>
<b>6 Implementation</b>	<b>2</b>

## 3 PIN Diagram

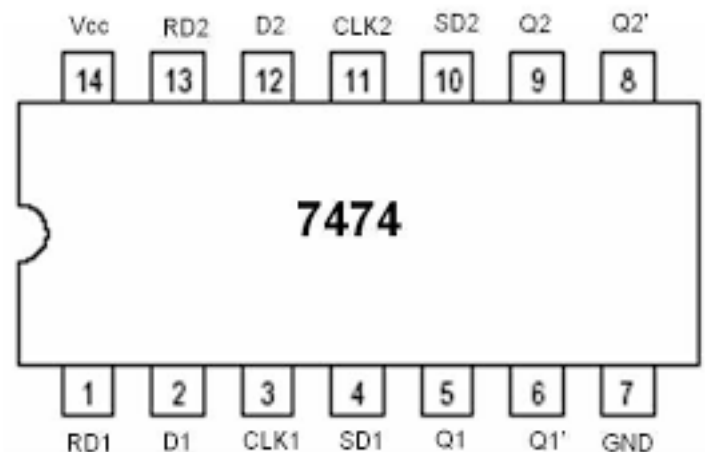


Figure.a

## Abstract

This manual explains about 4-bit shift register through 7474 IC in Arduino :

## 1 Introduction

### 1.1 7474 IC:

This IC contains 2 D-flip flops.

For this section total of 4 flip-flops(2 ICs) are required since we need to design a 4-bit shift register.

### 1.2 Arduino:

In Arduino Uno we generate the clock pulse which is given to the each and every flip-flop by default.

We take 5 volts and Ground as the supply to the bread board from the Arduino board.

## 4 Truth Table

D1	Q1=D2	Q2=D3	Q3=D4	Q4
0	0	0	0	0
1	1	0	0	0
1	1	1	0	0
0	0	1	1	0
1	1	0	1	1
0	0	1	0	1
0	0	0	1	0
0	0	0	0	1
0	0	0	0	0

Truth table for 1011

## 2 Components

Component	Values	Quantity
Arduino	UNO	1
JumperWires	M-M	20
Breadboard		1
IC	7447	2


## 5 Circuit Diagram

**shift-register** It has 4 D-flip flops.

It takes 1 input that is D1.

It has 4 outputs i.e Q1, Q2, Q3 and Q4.

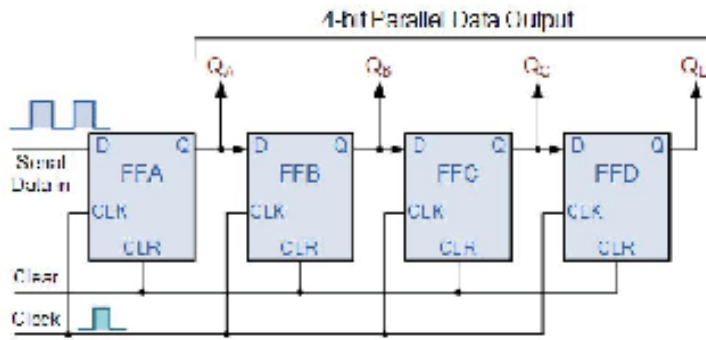By default it takes the input from LSB to MSB.



## 6 Implementation

Ard	D13	D13				Vcc	Vcc	Vcc	Vcc	Vcc	Gnd				
7474	3	11	5-12	9		1	4	10	13	14	7	5	9		
7474	3	11		2	5-12	1	4	10	13	14	7			5	9
LED												led1	led2	led3	led4

Connections

- Problem-1** 1. Connect the circuit as per the above table.  
2. Execute the circuit using the below code.

<https://github.com/siva-krishna-IITH-2022/fwc-assign/Assignment-1/IDE/codes>

- Problem-2** 1. Same circuit can be implemented by connecting a,b,c and d terminals of seven segment display to the Q1, Q2, Q3 AND Q4 respectively instead of using 4 LEDs.  
2. Execute the circuit using the above code.